

[B19EC2101]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech I Semester (R19) Regular Examinations
ELECTRONIC DEVICES AND CIRCUITS
Common to ECE & EEE


MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

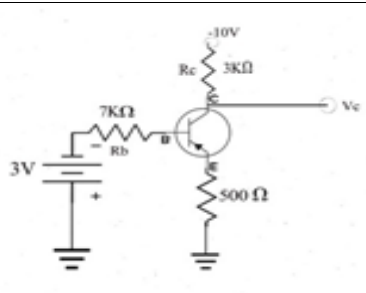			CO	KL	M
		UNIT-I			
1.	a).	Discuss in detail the various current components in a p-n junction diode.	CO1	K2	7
	b).	A Silicon diode operates at a forward voltage of 0.4 V. Calculate the factor by which the current will be multiplied when the temperature is increased from 25 degree centigrade to 150 degree centigrade.	CO1	K3	8
		OR			
2.	a).	With a neat diagram, explain the operation of a full wave rectifier and obtain expressions for ripple factor and efficiency.	CO1	K4	7
	b).	Distinguish between Zener breakdown and Avalanche breakdown.	CO1	K5	8
		UNIT-II			
3.	a).	Explain input and output characteristics of the transistor in CE configuration with a neat sketch.	CO1	K2	7
	b).	Compare CE, CC and CB configurations of a transistor.	CO1	K5	8
		OR			
4.	a).	Explain the early effect and its consequences in the Common base transistor.	CO1	K2	7
	b).	 For the circuit shown, $\beta_{dc} = 100$ and $V_{BE} = 0.8V$. (i). Find if the transistor is in cut off, saturation or active region. (ii). Find the voltage (V_c). (iii). Find the minimum value of R_b for which the transistor operates in an active region.	CO1	K3	8
		UNIT-III			
5.	a).	Explain how self-bias circuit improves stability of operating point and obtain an expression for the stability factor 'S' for the self-bias circuit	CO2	K4	7

	b).	Explain how diodes can be used to compensate against variations in V_{BE} and I_{CO} due to change in temperature.	CO2	K2	8
		OR			
6.	a).	A transistor with $\beta = 100$ is to be used in Common Emitter Configuration with collector to base bias. $R_E = 1\text{ K}\Omega$, $V_{CC} = 10\text{V}$. Assume $V_{BE} = 0.7\text{V}$. Choose R_B so that the quiescent collector to emitter voltage is 4V . Find Stability Factor S .	CO2	K3	7
	b).	Explain thermal runaway and thermal stability in transistors.	CO2	K2	8
		UNIT-IV			
7.	a).	Compare JFET and BJT.	CO1	K5	7
	b).	Draw the basic structure of N- channel JFET and explain the operation with the help of characteristic curves.	CO1	K2	8
		OR			
8.	a).	Explain the construction and operation of Enhancement MOSFET with drain and transfer characteristics.	CO1	K2	7
	b).	A JFET is to be connected in a circuit with a drain load resistor of $4.7\text{ k}\Omega$, and a supply voltage of $V_{DD} = 30\text{V}$. V_D is to be approximately 20V , and is to remain constant within $\pm 1\text{ V}$. Design a suitable self-bias circuit.	CO2	K3	8
		UNIT-V			
9.	a).	Derive expressions for current gain, Voltage gain, Input impedance and Output impedance of a generalized transistor amplifier using h-parameters.	CO3	K4	7
	b).	Explain the frequency response of the CE amplifier with a neat sketch.	CO3	K2	8
		OR			
10.	a).	Discuss the effect of bypass and coupling capacitors in CE amplifiers.	CO3	K2	7
	b).	Draw and explain a hybrid π - model of a transistor used at high frequencies.	CO3	K2	8

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19EC2101]

[B19EC2102]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech I Semester (R19) Regular Examinations
SWITCHING THEORY AND LOGIC DESIGN
Electronics and Communication Engineering

MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

			CO	KL	M
		UNIT-I			
1.	a).	Convert 1096_{10} into Binary, Octal, Hexadecimal, BCD and Excess-3.	1	3	8
	b).	Simplify the following functions by using basic Boolean laws i) $\overline{XZ} + XYZ + X\overline{Z} = Y$ ii) $A\overline{B}C + (\overline{B} + \overline{C})(\overline{B} + \overline{D}) + (A + C + D) = Y$	1	2	7
		OR			
2.	a).	Explain how you can detect single error occurred during transmission in a 7 bit Hamming code word with an example.	1	3	8
	b).	i) Prove that $\overline{(A \oplus B)} \oplus C = A \oplus (B \oplus C)$ ii) Simplify $\overline{A}B + ABD + \overline{A}\overline{B}CD + BC = Y$	1	2	7
		UNIT-II			
3.	a).	Express the following in SOP and POS forms i) $(AB + C)(B + \overline{C}D)$ ii) $\overline{x} + x(x + \overline{y})(y + \overline{z})$	2	2	6
	b).	Simplify using K-Map $f(A,B,C,D) = \sum m(0,1,3,7,8,12) + \sum d(5,10,13,14)$ and draw the corresponding circuit with only NAND gates.	2	3	9
		OR			
4.	a).	Simplify the given function by using K-map $f(A,B,C,D) = \sum m(0,1,4,5,7,11,15) + \sum d(10,13)$	2	2	6
	b).	Find Prime Implicants of $f(w,x,y,z) = \sum m(1,4,6,7,8,9,10,11,15)$ by using Quine – McCluskey method.	2	3	9
		UNIT-III			
5.	a).	Design an 8:1 Multiplexer with only NAND Gates.	3	4	8
	b).	Implement the given functions by using a 3 to 8 Decoder and logic Gates. (i) $f_1(A,B,C) = \sum m(0,1,5,7)$ (ii) $f_2(A,B,C) = \sum m(1,3,5,7)$	3	3	7
		OR			
6.	a).	Design and draw a BCD to 7 segment Decoder circuit for active	3	4	8

		low outputs.																																																									
	b).	What is the function of priority encoder? Design a 3bit priority encoder.	3	3	7																																																						
		UNIT-IV																																																									
7.	a).	Convert D-FF into JK-FF.	3	4	8																																																						
	b).	What is a race around problem in a JK flip-flop and explain the method to avoid it by using Master Slave JK-FF.	3	3	7																																																						
		OR																																																									
8.	a).	Draw a 3-bit right shift register and explain the modes SIPO, SISO, PIPO and PISO.	3	3	7																																																						
	b).	Design Mod-5 Ring counter and draw its output waveforms.	3	4	8																																																						
		UNIT-V																																																									
9.	a).	Explain difference between synchronous and asynchronous circuits.	4	3	7																																																						
	b).	Design a Sequence detector which produces an output 0 every time the sequence 0101 is detected, an output 1 at all other times. Assume that overlapping sequence is allowed. Use D-FFs in your design.	4	4	8																																																						
		OR																																																									
10.	a).	Design a synchronous sequential circuit using D-FFs for the given state table. <table><tr><th colspan="2" rowspan="2">Present State</th><th colspan="4">Next State</th><th colspan="2">Output</th></tr><tr><th colspan="2">X=0</th><th colspan="2">X=1</th><th>X=0</th><th>X=1</th></tr><tr><th>A</th><th>B</th><th>A</th><th>B</th><th>A</th><th>B</th><th>A</th><th>B</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr></table>	Present State		Next State				Output		X=0		X=1		X=0	X=1	A	B	A	B	A	B	A	B	0	0	0	0	0	1	0	0	0	1	0	0	1	1	1	0	1	0	0	0	1	0	1	0	1	1	0	0	1	0	1	0	4	4	8
Present State		Next State				Output																																																					
		X=0		X=1		X=0	X=1																																																				
A	B	A	B	A	B	A	B																																																				
0	0	0	0	0	1	0	0																																																				
0	1	0	0	1	1	1	0																																																				
1	0	0	0	1	0	1	0																																																				
1	1	0	0	1	0	1	0																																																				
	b).	What is lockout in counters? Design a Mod-10 synchronous counter by using D-Flip- Flops.	4	3	7																																																						

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19EC2102]


[B19EC2103]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE(A)
II/IV B.Tech I Semester (R19) Regular Examinations
SIGNALS AND SYSTEMS
ELECTRONICS AND COMMUNICATION DEPARTMENT
MODEL QUESTION PAPER


TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

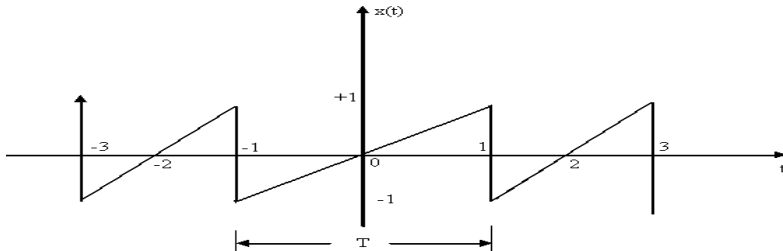			CO	KL	M
		UNIT-I			
1.	a).	Explain all classification of signals with examples for each category.	1	2	8
	b).	Determine the power and RMS value of the following signals $1 . x(t) = 5 \cos(50t + 3)$ $2 . x(t) = 10\cos(5t)\cos(10t)$	1	3	7
		OR			
2.	a).	Determine whether the following systems are time invariant or not. $1 . y(t) = x(t)$ $2 . y(n) = x(2n)$	1	3	8
	b).	Prove the energy of the power signal is infinite over infinite time.	1	2	7
		UNIT-II			
3.	a).	Find the trigonometric Fourier series for the periodic signal $x(t)$ as shown in figure below 	2	3	7
	b).	State and prove parseval's relation of Fourier series.	2	2	8
		OR			
4.	a).	State and prove the time shifting and time scaling properties of CTFS.	2	2	7
	b).	Explain Dirichlet conditions on Convergence of Fourier Series.	2	2	8
		UNIT-III			
5.	a).	State and prove the differentiation in the frequency domain property of CTFT.	3	2	8
	b).	Find $x(t)$ from $X(j\omega) = 1/(1+j\omega)^2$	3	3	7
		OR			

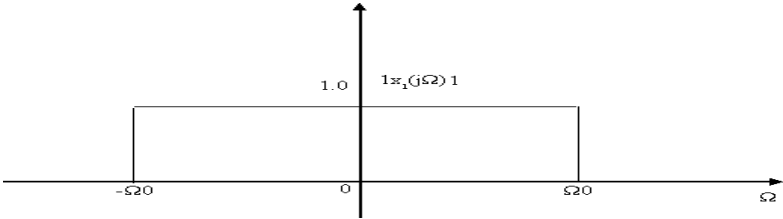6.	a).	Find the inverse Fourier transform of $X(j\Omega)$ for the spectra shown in figure below.	3	3	7
					
	b).	Find the Fourier transform of the following: 1. $e^{at}u(-t)$ 2. $te^{-at}u(t)$	3	3	8
		UNIT-IV			
7.	a).	State and prove the final value theorem of Laplace transform.	4	2	8
	b).	Compute the initial and final values for $X(S) = (2S+5)/(S(S+3)(S+4)^2)$	4	2	7
		OR			
8.	a).	Explain ROC properties of Laplace transforms.	4	2	8
	b).	Determine the bilateral Laplace transform and ROC for the following signals. (i) $e^{-2t}u(t-2)$ (ii) $e^{-4 t }$	4	3	7
		UNIT-V			
9.	a).	Find the inverse z-transform of the following: 1. $X(z) = \frac{1}{(1+3Z^{-1}+2Z^{-2})}$ ROC: $\text{mod}(Z) > 2$ 2. $X(z) = \frac{(Z+1)}{(4+35+Z^2)}$ ROC: $\text{mod}(Z) < 2$	5	3	7
	b).	Solve the following difference equation for $y(n)$ using z-transform for the specified Initial condition. $y(n) - y(n-1) + \frac{1}{4}(y(n-2)) = X(n) : n > 0$ where $X(n) = 2\left(\frac{1}{8}\right)^n$; $y(-1) = 2$; $y(-2) = 4$.	5	3	8
		OR			
10.	a).	A signal $x(t) = \sin c(150\pi t)$ is sampled at a rate of (i) 100Hz (ii) 200 Hz (iii) 300Hz. For each of these cases, explain if you can recover the signal $x(t)$ from the sampled signal.	6	3	7
	b).	Find the z-transform and ROC for the following: 1. $x(n) = a^n u(n)$ 2. $x(n) = -b^n u(-n-1)$.	5	3	8

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19EC2104]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech I Semester (R19) Regular Examinations
PROBABILITY THEORY & RANDOM PROCESSES
Electronics and Communication Engineering

MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

			CO	KL	M
		UNIT-I			
1.	a).	State and prove Bayes theorem.	CO1	K2	8
	b).	A single card is drawn from a 52 card deck (i) What is the probability that the card is a jack? (ii) What is the probability that the card will be a 5 (or) smaller? (iii) What is the probability that the card is a red 10?	CO1	K3	7
		OR			
2.	a).	State and prove Addition theorem of probability.	CO1	K2	8
	b).	In a classroom, 70% are above average, 20% are average and 10% are below average. Suppose that 20% of above average, 10% of average and 20% of below average students fail in a subject. What is the probability that a randomly selected student is an average student who failed?	CO1	K3	7
		UNIT-II			
3.	a).	Define Distribution and Density functions. List the properties of them. Prove any one property of each.	CO2	K2	7
	b).	A random variable X has a probability density function $f_X(x) = \frac{c}{x^2+1} \quad -\alpha < x < \alpha$ Find the constant 'c' and also find the probability distribution function of the random variable X.	CO2	K3	8
		OR			
4.	a).	The joint probability density function of two random variables x and y is given by $f_{XY}(x,y) = e^{-(x+y)} \quad \text{If } x \geq 0, y \geq 0,$ $= 0 \quad \text{otherwise.}$ Find the marginal density functions of x and y. Also prove that x and y are independent.	CO2	K3	8
	b).	A random variable X has a Gaussian density function with mean '0' and variance '1'. Find the probability density function of the random variable Y defined as $Y = X^2$.	CO2	K3	7
		UNIT-III			

5.	a).	State and prove Chebyshev's inequality .	CO3	K2	7
	b).	A random variable has a probability density function $f_X(x) = \frac{5}{4}(1 - x^4) \quad \text{for } 0 < x \leq 1,$ $= 0 \quad \text{elsewhere}$ Find (i) E(X) (ii) E (4X+2) (iii) E(X ²).	CO3	K3	8
		OR			
6.	a).	Compute the characteristic function for a random variable X with $f_X(x) = \frac{1}{2} e^{- x }, -\alpha \leq x \leq \alpha$	CO3	K3	7
	b).	State and Prove Central Limit Theorem.	CO3	K2	8
		UNIT-IV			
7.	a).	Define Autocorrelation and power spectral density for a random process. List their Properties.	CO4	K2	8
	b).	Determine the PSD of a stationary process whose autocorrelation is given by $R_{XX}(\tau) = \sigma^2 e^{-\alpha \tau }$	CO4	K3	7
		OR			
8.	a).	Prove that the random process is wide sense stationary $X(t) = A \cos(\omega_0 t + \theta)$ where A, ω_0 are constants and θ is uniformly distributed random variable on the interval (0, 2 π).	CO4	K3	8
	b).	Distinguish between stationary and Ergodic random processes.	CO4	K3	7
		UNIT-V			
9.	a).	Find the input autocorrelation function, output autocorrelation function and output spectral density of RC low pass filter, when the filter is subjected to a white noise of spectral density $N_0/2$.	CO5	K5	8
	b).	Show that the Narrow band noise process can be expressed as In-phase and Quadrature components.	CO5	K2	7
		OR			
10.	a).	What is Low pass and Band pass noise representation and write their properties?	CO5	K2	7
	b).	Write short notes on (i) Poisson Process (ii) Gaussian Process	CO5	K2	8

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS




[B19EE2105]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II B. Tech I Semester (R19) Regular Examinations
NETWORK ANALYSIS
Electronics and Communication Engineering
MODEL QUESTION PAPER




TIME: 3Hrs.

Max. Marks: 75M





Answer **ONE Question** from **EACH UNIT**.


All questions carry equal marks.

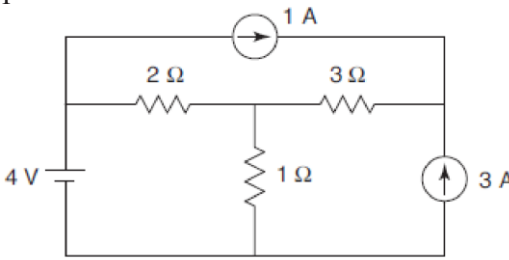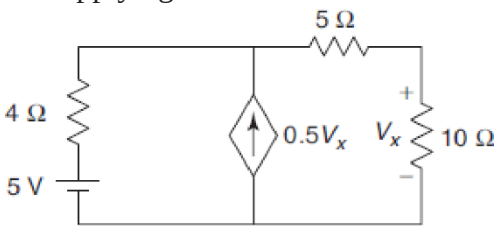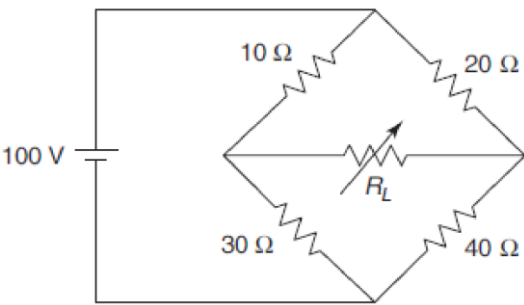			CO	PO	M
		UNIT-I			
1.	a).	Apply Super position theorem to find the current in the 1Ω resistor. 	CO1	PO1	7
	b).	Find the current through the 10Ω resistor for the network by applying thevenin's theorem. 	CO1	PO1	8
		OR			
2.	a).	Find the value of resistance R_L in the given network for maximum power transfer and calculate the maximum power by applying maximum power transfer principle. 	CO1	PO1	7

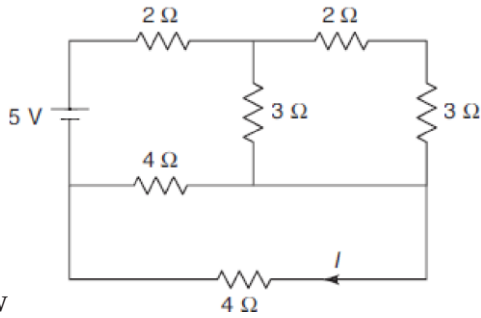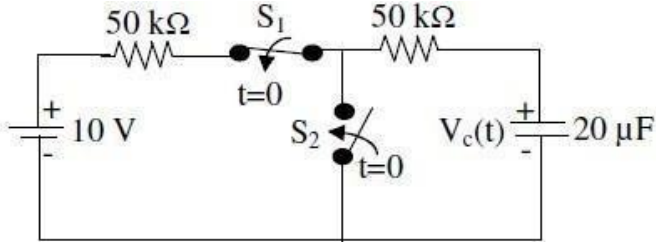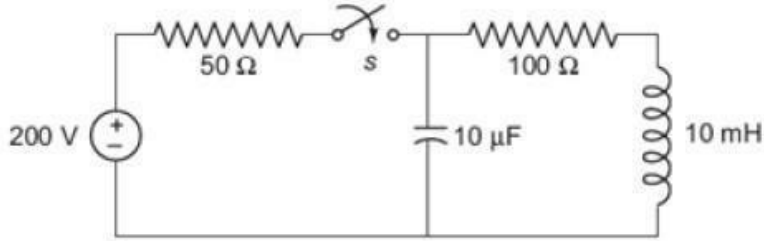	b).	Find the current I and verify reciprocity theorem for the network shown below	CO1	PO1	8
					
		UNIT-II			
3.	a).	Derive an expression for the current in an RC circuit excited by a unit step voltage. And draw the corresponding plot.	CO2	PO1	7
	b).	In the circuit of figure, switch S_1 has been closed for a long time while switch S_2 has been open for a long time. At $t=0$, switch S_1 opens and switch S_2 closes. Determine the value of voltage $V_c(t)$ for all $t>0$.	CO2	PO2	7
					
		OR			
4.	a).	Derive an expression for the current in an RL circuit excited by a unit step voltage.	CO2	PO1	8
	b).	When the switch is closed at $t = 0$, determine the transient current through inductor for the network shown in below Figure. Assume that initial current through the inductor is zero.	CO2	PO2	7
					
		UNIT-III			
5.	a).	Determine the current through $(4 - j8) \Omega$ branch in the circuit shown in Figure using Thevenin's theorem and Norton's theorem.	CO3	PO1	

	b).	An R-L-C circuit has the following values: $R = 40\Omega$, $C = 0.01\mu\text{F}$, $L = 100\text{ mH}$ and the resistance of the coil is 10Ω. An input voltage 120 mV of variable frequency is appearing at the input. The output is taken out from the L-C combination. Calculate the output voltage at resonance. Further, calculate the bandwidth.	CO3	PO1	8
		OR			
6.	a).	Find the current through 6Ω resistor shown in Figure by applying mesh analysis.	CO3	PO1	7
	b).	A series RLC circuit with $R = 10\text{ ohms}$, $L = 0.4\text{ H}$ and $C = 50\mu\text{F}$ has applied voltage of 200V with variable frequency. Calculate the resonant frequency, current at resonance, voltage across R, L and C. Also calculate the Q-factor, upper and lower half power frequencies and bandwidth.	CO3	PO1	8
		UNIT-IV			
7.	a).	Calculate Y-parameters for the network shown in below.	CO4	PO1	7

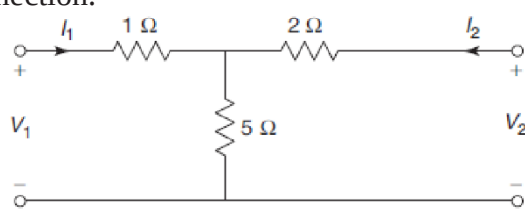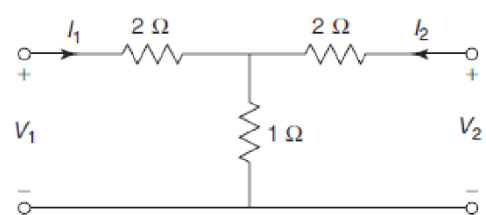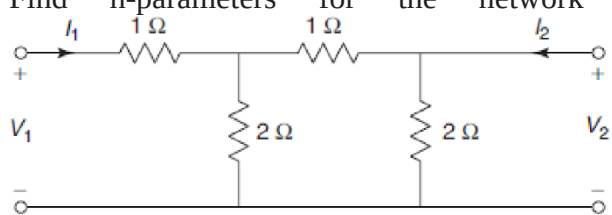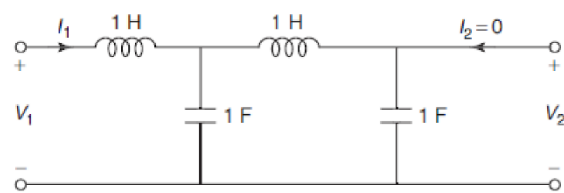	b).	Two identical sections of the network shown in Fig., are connected in cascade. Obtain the transmission parameters of the overall connection.	CO4	PO1	7
					
		OR			
8.	a).	Two identical sections of the network shown in below fig., are connected in series. Obtain Z-parameters of the overall connection.	CO4	PO1	7
					
	b).	Find h-parameters for the network shown below.	CO4	PO1	8
					
		UNIT-V			
9.	a).	Find the network functions V_2/V_1 , V_2/I_1 and V_2/I_2 for the network shown in below	CO5	PO1	7
		 fig.,			
	b).	Find the function $v(t)$ using the pole-zero plot of following function	CO5	PO1	7
		$V(s) = \frac{(s+2)(s+6)}{(s+1)(s+5)}$			
		OR			

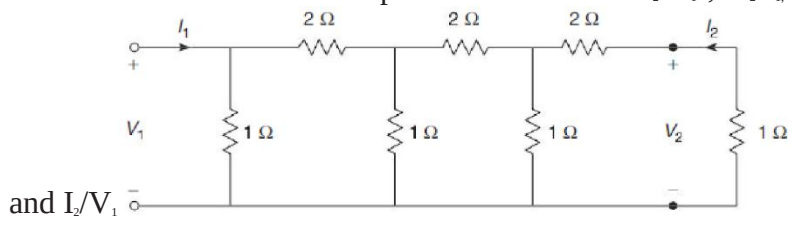10.	a).	For the below resistive two-port network find V_2/V_1, V_2/I_1, I_2/I_1  and I_2/V_1	CO5	PO1	8
	b).	The denominator of a network function is expressed as a polynomial For what value of K, the system will be stable? $Q(s) = s^3 + 2s^2 + 3s + K$	CO5	PO2	7

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19CS2108]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II B. Tech I Semester (R19) Regular Examinations
DATA STRUCTURES
COMMON TO ECE & EEE
MODEL QUESTION PAPER



TIME: 3Hrs.

Max. Marks: 75M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

UNIT-I				CO-PO	K
1.	(a)	Applying stack operations Write an algorithm for postfix evaluation and Applying Postfix Evaluation algorithm Evaluate the following postfix expression. 2 3 8 5 1 + - \$ * 9 6 - *	8M	CO1-PO1	K3
	(b)	Construct a non-recursive algorithm for binary search. Write Non-Recursive algorithms for finding the n th Fibonacci number.	7M	CO1-PO1	K3
(OR)					
2.	(a).	Identify C routines for primitive operations on stack	8M	CO1-PO1	K3
	(b)	Applying stack operations Write an algorithm for infix to postfix. Apply algorithm Convert the following infix expression to postfix expression. A + (B * C - (D / E \$ F) * G) * H	7M	CO1-PO1	K3
UNIT-II					
3.	(a).	Apply Linked list to perform stack operations.	8M	CO2-PO1	K3
	(b)	Apply Double Linked list to perform insertion operation.	7M	CO2-PO1	K3
(OR)					
4.		Build an algorithm to find transpose of the given sparse matrix and also implement it by using a c program.	15 M	CO2-PO1	K3
UNIT-III					
5.		Explain Binary tree traversal techniques and Construct a Binary Tree from inorder 4,8,2,5,1,6,3,7 and post order 8,4,5,2,6,7,3,1.	15 M	CO3-PO1	K3
(OR)					
6.	(a).	Construct a Threaded binary tree by taking Binary Tree example	8M	CO3-PO1	K3
	(b)	Construct Min Heap an Max Heap for given Input 35 33 42 10 14 19 27 44 26 31	7M	CO-PO1	K3
UNIT -IV					
7.	(a).	Explain warshall's algorithm and identify the transitive closure of a graph with an example.	8M	CO3-PO1	K3

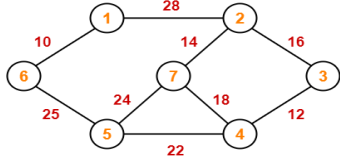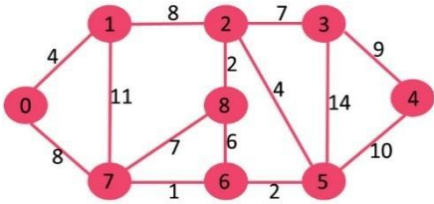	(b) .	Apply BFS traversal of a graph with an example	7M	CO3 -PO1	K3
(OR)					
8.	(a)	Construct Minimum Spanning Tree by Kruskal algorithm 	8M	CO3 -PO1	K3
	(b)	Construct Minimum Spanning Tree by Prim's Algorithm 	7M	CO3 -PO1	K3
UNIT-V					
9.		Analyse and sort the given input elements using quick sort technique 52, 37, 63, 14, 17, 8, 6, 25	15 M	CO4 -PO2	K4
(OR)					
10 .		Analyse with binary search technique to identify the element 65 in the give list of elements: 10,20,40,65,75,87,99,	15 M	CO4 -PO2	K4

[B19EC2201]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech I Semester (R19) Regular Examinations
ELECTRONIC CIRCUIT ANALYSIS
Department of Electronics and Communication Engineering

MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

			CO	KL	M
		UNIT-I			
1.	a).	Show that the low band gain of an FET RC coupled amplifier at low frequency is $(-g_m R_o R_s / (R_o + R_s + 1/j\omega C_c))$	3	4	8M
	b).	A transistor is connected as a CE amplifier with load resistance of $10K\Omega$. The parameters are $h_{ie}=5K\Omega$ and $h_{fe}=330$. Calculate the overall gain for mid frequency range when four such stages are connected in cascaded RC coupling. Assume $R_s=0$.	2	3	7M
		OR			
2.	a).	Explain what you understand by the term bandwidth shrinkage factor as applied to cascaded RC stages. Determine the expression for the same.	2	3	7M
	b).	Determine the expression for short circuit current Gain-Bandwidth product of a CE amplifier.	2	3	8M
		UNIT-II			
3.	a).	Determine expressions for input impedance and output impedance in case of a voltage series feedback topology.	2	3	8M
	b).	An amplifier gain change by $\pm 10\%$ using negative feedback amplifier is to be modified to yield gain of 100 with 0.1% variation. Calculate the required loop gain and amount of negative feedback.	2	3	7M
		OR			
4.	a).	Determine the expressions for input impedance and output impedance for a current shunt feedback topology.	2	3	8M
	b).	Evaluate the voltage gain, input impedance and output impedance of an amplifier with feedback for voltage series feedback having $A=100$, $R_i=10K\Omega$, $R_o=20K\Omega$ and $\beta=0.1$.	3	4	7M
		UNIT-III			
5.	a).	Determine the expression for the frequency of oscillations of an RC- Phase shift oscillator.	2	3	7M

	b).	In a Colpitts oscillator $C_1 = 0.001 \text{ mF}$ and $C_2 = 0.01 \text{ mF}$ and $L = 5 \text{ mH}$. Evaluate (i).Frequency of oscillations (ii) If 'L' is doubled, find the new frequency.	3	4	8M
		OR			
6.	a).	Discuss about Crystal oscillators with neat diagrams and necessary equations.	1	2	6M
	b).	Demonstrate how the oscillations are built up in the Hartley oscillator with a neat circuit diagram and also derive the expression for the same.	2	3	9M
		UNIT-IV			
7.	a).	Compare single tuned and stagger tuned amplifiers.	1	2	6M
	b).	Classify the Power amplifiers and Show that the efficiency of a transformer coupled class A power amplifier is 50%	2	3	9M
		OR			
8.	a).	Sketch and explain the neat circuit diagram of a Single tuned amplifier and deduce the expression for gain.	2	3	8M
	b).	Explain how even harmonic distortion is reduced in a Class-A push-pull power amplifier.	1	2	7M
		UNIT-V			
9.	a).	With the help of neat diagrams, explain the following applications using Op-Amp. (i) Non-Inverting amplifier. (ii) Summing amplifier	1	2	8M
	b).	Explain the concept of "Virtual ground" for OP-AMPs and derive an expression for closed loop gain of inverting configuration of OP-AMP	2	3	7M
		OR			
10.	a).	Discuss about the following OP-AMP parameters: (i) CMRR, (ii) PSRR and (iii) I/P Bias Current	1	2	7M
	b).	Analyze and design an OP-AMP circuit to give an output $V_o = \frac{3}{4} V_1 + \frac{5}{6} V_2 + \frac{6}{7} V_3$, where $V_1=V_2=V_3=1 \text{ V}$	3	4	8M

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19EC2201]

[B19EC2202]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech II Semester (R19) Regular Examinations
ELECTROMAGNETIC WAVES AND TRANSMISSION LINES
Electronics and Communication Engineering

MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

			CO	KL	M
		UNIT-I			
1.	a).	A charge $Q = -10\text{nc}$ is at the origin in free space. If the x -component of $\mathbf{E}$ is to be zero at the point (3,1,1), determine the value Q , which should be kept at the point (2,0,0).	1	K4	7
	b).	State Gauss's law. Deduce the expression for Electric field due to an infinite line charge.	1	K3	8
		OR			
2.	a).	Define conduction current density. Derive the expression for continuity equation.	1	K3	8
	b).	The dielectric medium1 has permittivity $\epsilon_{r1} = 2$, dielectric medium2 has permittivity $\epsilon_{r2} = 4$ and electric field in medium1 is $\mathbf{E}_1 = 5\mathbf{a}_x + 3\mathbf{a}_y - 13/\mathbf{z}\mathbf{a}_z$ v/m. Determine electric field in medium2 $\mathbf{E}_2$	1	K4	7
		UNIT-II			
3.	a).	Explain about Biot Savart's law in detail.	1	K3	7
	b).	The Magnetic field intensity in a region of space is $\mathbf{H} = (x+2y)/z^2\mathbf{a}_y + 2/z\mathbf{a}_x$ A/M. Determine $\mathbf{J}$ and also the total current passing through the surface $Z=4$, $1 \leq X \leq 2$, $3 \leq Y \leq 5$.	1	K4	8
		OR			
4.	a).	Determine the magnetic potential at a distant point due to a small circular loop of radius a carrying a current I amperes.	1	K4	7
	b).	Explain about the Force due to the magnetic field on a moving charge and on a current element.	1	K3	8
		UNIT-III			

5.	a).	Deduce the expressions for Maxwell's equations in both differential and integral form.	2	K3	8
	b).	Given $\mathbf{E}=10\sin(\omega t-\beta z)\mathbf{a}_z$ V/m in free space, determine $\mathbf{D}$, $\mathbf{B}$ and $\mathbf{H}$.	2	K4	7
		OR			
6.	a).	Deduce the boundary conditions for $\mathbf{E}$, $\mathbf{H}$, $\mathbf{D}$ and $\mathbf{B}$ at the interface between two different dielectric media.	2	K3	8
	b).	A medium is characterized by $\sigma = 0$, $\mu = 2\mu_0$, and $\epsilon = 5\epsilon_0$. If $\mathbf{H} = 2\cos\{(\omega t - 3y)\}\mathbf{a}_z$, A/m, calculate ω and $\mathbf{E}$.	2	K4	7
		UNIT-IV			
7.	a).	Define uniform plane wave. Deduce the expression for intrinsic impedance of free space.	3	K3	8
	b).	State wave propagation characteristics of good conductors. A medium is defined by $\sigma = 5.8 \times 10^7$ mho/m, $\epsilon_r = 1$, $\mu_r = 1$, supports a uniform plane wave of frequency 60Hz. Determine the attenuation constant, propagation constant, intrinsic impedance, wavelength and phase velocity.	3	K4	7
		OR			
8.	a).	List different types of polarization. Explain about circular polarization of a uniform plane wave.	3	K3	7
	b).	Derive the expression for reflection and transmission coefficients, when a uniform plane wave incident normally on the surface of a perfect dielectric.	3	K3	8
		UNIT-V			
9.	a).	A distortionless line has $Z_0 = 50\Omega$, $\alpha = 20$ m Np/m, $V = 0.6C$, where C is the speed of light in vacuum. Compute R , L , G , C and λ at 100 MHz.	4	K3	7
	b).	Derive the input impedance of a Transmission line in terms of characteristic impedance.	4	K3	8
		OR			
10.	a).	A rectangular waveguide has cross-sectional area of $2.29 \times 1.45 \text{ cm}^2$ and operating frequency is 10 GHz. Calculate (a) free space wavelength (b) cut-off wavelength (c) cut-off frequency (d) angle of incidence (e) guide wavelength (f) phase velocity (g) phase drift constant and wave impedances of the waveguide (TE and TM).	4	K3	8

	b).	Explain the reason for inability of rectangular waveguide to allow TEM mode propagation.	4	K3	7
--	------------	--	----------	-----------	----------

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19 EC2203]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech II Semester (R19) Regular Examinations
ANALOG COMMUNICATIONS
Department of Electronics and Communication Engineering

MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 70 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

			CO	KL	M
		UNIT-I			
1.	a)	Explain the AM diode detector demodulator with a neat diagram.	CO1	K2	7
	b)	Explain the generation of DSB-SC with the Balanced modulator method.	CO1	K2	7
		OR			
2.	a)	Explain advantages of SSB system. Describe a method of generating an SSB signal.	CO1	K2	7
	b)	Explain Vestigial Side Band Modulation.	CO1	K2	7
		UNIT-II			
3.	a)	Define frequency deviation and phase deviation in Frequency Modulation and differentiate between NBFM and WBFM.	CO2	K3	7
	b)	In a FM system when the audio frequency is 500Hz and the AF voltage is 2.4 V, the frequency deviation is 4.8 kHz. If the AF voltage is increased to 7.2V, what is the new deviation? If the AF voltage is raised to 10V, while audio frequency is dropped to 200Hz, what is the deviation? Find the modulation index in each case.	CO2	K3	7
		OR			
4.	a)	Describe the operation of a phase locked loop FM demodulator with a neat diagram.	CO2	K2	7
	b)	Draw the block diagram of an Indirect method of FM generation and explain.	CO2	K2	7
		UNIT-III			
5.	a)	Derive the expression for signal -to-noise ratio in DSB-SC system.	CO3	K3	8
	b)	Explain sources of Noise.	CO3	K2	6
		OR			
6.	a)	Derive the expression for signal -to-noise ratio in FM systems.	CO3	K3	10

	b)	Explain Threshold in FM.	CO3	K2	4
		UNIT-IV			
7.	a)	Draw the block Diagram of AM transmitter and Explain.	CO4	K2	8
	b)	Explain Pre-Emphasis & De-emphasis.	CO4	K2	6
		OR			
8.	a)	Draw the block diagram of FM transmitter and Explain.	CO4	K2	7
	b)	Draw the block diagram of an SSB transmitter and Explain.	CO4	K2	7
		UNIT-V			
9.	a)	Explain the principle of operation of a super heterodyne radio receiver.	CO5	K2	8
	b)	What are the factors that govern the choice of Intermediate frequency?	CO5	K2	6
		OR			
10	a)	Distinguish between AGC and Delayed AGC with help of neat circuit diagrams.	CO5	K4	7
	b)	Define Image frequency and Image frequency Rejection Ratio.	CO5	K2	7

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19 EC2203]

[B19EC2204]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech II Semester (R19) Regular Examinations
COMPUTER ARCHITECTURE AND ORGANIZATION
Electronics and Communication Engineering

MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

			CO	K L	M																		
		UNIT-I																					
1.	a).	Explain the operation of a 4-bit adder-subtractor with a neat diagram.	CO 1	K 3	7																		
	b).	Design a common bus system with multiplexers to connect four 4 bit registers A,B,C,D. How this can be modified with the help of a three state buffer.	CO 1	K 3	8																		
		OR																					
2.	a).	Explain in detail the operation of one stage arithmetic logic shift unit by using a function table for each input.	CO 1	K 3	8																		
	b).	The adder- subtractor circuit has following values for input mode M and data inputs A and B. In each case, determine the values of the outputs: S ₃ , S ₂ , S ₁ , S ₀ and C ₄ .	CO 1	K 3	7																		
		<table><tr><td>M</td><td>A</td><td>B</td></tr><tr><td>0</td><td>0111</td><td>0110</td></tr><tr><td>0</td><td>1000</td><td>1001</td></tr><tr><td>1</td><td>1100</td><td>1000</td></tr><tr><td>1</td><td>0101</td><td>1010</td></tr><tr><td>1</td><td>0000</td><td>0001</td></tr></table>	M	A	B	0	0111	0110	0	1000	1001	1	1100	1000	1	0101	1010	1	0000	0001			
M	A	B																					
0	0111	0110																					
0	1000	1001																					
1	1100	1000																					
1	0101	1010																					
1	0000	0001																					
		UNIT-II																					
3.	a).	Explain about Timing and Control Unit design.	CO 2	K 2	7																		
	b).	With the help of a flowchart explain the operation of a basic computer during 1. Instruction cycle 2. Interrupt cycle	CO 2	K 3	8																		
		OR																					
4.	a).	Explain in detail about basic instruction formats with examples.	CO 2	K 3	7																		
	b).	With the help of a diagram explain the functions of the basic computer registers connected to a common bus.	CO 2	K 3	8																		
		UNIT-III																					

5.	a).	Write the merits and demerits of a micro programmed control unit compared to a hardwired control unit.	CO 3	K 2	7
	b).	Explain the concept of microprogramming in detail with the help of an example.	CO 3	K 4	8
		OR			
6.	a).	With an example, explain various addressing modes and write how to calculate the address in each case.	CO 3	K 4	8
	b).	What are the characteristics of a RISC processor? What is a CISC processor?	CO 3	K 2	7
		UNIT-IV			
7.	a).	Explain Daisy Chain Interrupt Mechanism. List the advantages and disadvantages in this scheme.	CO 4	K 2	7
	b).	With the help of block diagram and truth table explain the operation of an I/O interface unit`	CO 4	K 3	8
		OR			
8.	a).	Show internal configuration of DMA and explain its operation in a computer for read and write modes.	CO 4	K 3	8
	b).	Explain the operation of Asynchronous Communication Interface.	CO 4	K 2	7
		UNIT-V			
9.	a).	A system employs RAM chips of 256bytes and ROM chips of 1024bytes. It needs 2KB RAM, 4KB ROM and four interface units with four registers each and memory mapped I/O used. The two highest order bits of the address bus are 00 for RAM, 01 for ROM and 10 for interface registers. Draw a memory address map for the system	CO 4	K 3	8
	b).	What is Cache memory and explain two mapping methods in implementation of Cache.	CO 4	K 3	7
		OR			
10.	a).	Explain Memory hierarchy and Differentiate between Main memory and Auxiliary memories	CO 4	K 2	7
	b).	Explain the following 1. Associative Memory 2. Virtual Memory	CO 4	K 2	8

CO-COURSE OUTCOME

KL-KNOWLEDGE LEVEL

M-MARKS

[B19EC2204]

[B19CS2209]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech II Semester (R19) Regular Examinations
OOPS THROUGH JAVA
Common to ECE & EEE
MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks:75

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

UNIT-I				CO	K
1.	(a).	Define an Array and explain different types of arrays. By applying the concept of an array find the largest element from a given set of elements in an array.	15 M	CO1 -PO1	K3
(OR)					
2.	(a).	Illustrate the differences between C, C++ and Java with a neat diagram	8M	CO1 -PO1	K3
	(b).	Illustrate the structure of a java program	7M	CO1 -PO1	K3
UNIT-II					
3.	(a).	Illustrate the concept of Inheritance and its different types with neat pictures.	8M	CO2 -PO2	K3
	(b).	Construct a sample java program of user choice which applies the functionality of inheritance.	7M	CO2 -PO2	K3
(OR)					
4.		Explain polymorphism and its types. Construct a java program which illustrates the functionality of method overloading and method overriding.	15 M	CO2 -PO2	K3
UNIT-III					
5.		Illustrate how to solve the problem of multiple inheritance in java with an example. Also differentiate between class and an interface.	15 M	CO3 -PO2	K3
(OR)					
6.	(a).	Interpret the concept of packages in java.	7M	CO3 -PO2	K3
	(b).	Construct a java program that shows the functionality of creating a public class in an already existing user defined package.	8M	CO3 -PO3	K3
UNIT -IV					
7.	(a).	Compare throw and throws in Exception Handling	8M	CO3 -PO2	K3
	(b).	Construct a java program which creates a user defined exception	7M	CO3 -PO3	K3
(OR)					
8.		Identify the different ways of creating a Thread in java programming, show with examples programs wherever necessary.	15 M	CO3 -PO3	K3

UNIT-V					
9.		Illustrate Life cycle of an applet. Construct a sample Applet program which displays current date.	15 M	CO4 -PO3	K3
(OR)					
10 .		Apply the concept of Event Handling and construct a java program which contains a button with name “day”,when clicked on it displays the current day.	15 M	CO4 -PO3	K3

[B19CS2209]

[B19HS2201]
SAGI RAMA KRISHNAM RAJU ENGINEERING COLLEGE (A)
II/IV B.Tech II Semester (R19) Regular Examinations
MANAGEMENT AND ORGANIZATIONAL BEHAVIOR

Common to ECE & EEE
MODEL QUESTION PAPER

TIME: 3Hrs.

Max. Marks: 75 M

Answer **ONE Question** from **EACH UNIT**.

All questions carry equal marks.

		CO	KL	M
	UNIT-I			
1.	Define Management and Explain its functions.	CO1	K2	15
	OR			
2.	Explain the principles of Management as outlined by Henry Fayol.	CO1	K2	15
	UNIT-II			
3.	Describe the functions performed by Human Resource Manager.	CO2	K2	15
	OR			
4.	Define Marketing, Explain in detail about Marketing mix.	CO2	K2	15
	UNIT-III			
5.	Explain about the importance of Mission, Goal, Objective and Strategy.	CO3	K2	15
	OR			
6.	What do you understand by SWOT analysis? Explain how it can be carried out.	CO3	K2	15
	UNIT-IV			
7.	What is Organisational Change and describe about the types of change.	CO4	K2	15
	OR			
8.	What is Motivation and Explain about Maslows Human Need Theory.	CO4	K2	15
	UNIT-V			
9.	Explain about the consequences of conflicts in an organisation.	CO5	K2	15
	OR			
10.	What is Stress & Describe about methods of managing Stress.	CO5	K2	15

[B19HS2201]